

FACULTY	AGRICULTURE, ENGINEERING AND NATURAL SCIENCES		
SCHOOL	ENGINEERING AND THE BUILT ENVIRONMENT		
DEPARTMENT	ELECTRICAL AND COMPUTER ENGINEERING		
SUBJECT	ANALOGUE ELECTRONICS II		
SUBJECT CODE	I3781CA		
DATE	MAY 2024		
DURATION	3 HOURS	MARKS	100

First Opportunity Examination

Examiner: MR. F.S. SHAFUDA

Internal Moderator: MR. F.M.S ABISAI

External Moderator: PROF. J AGAJO

This Exam consists of 3 pages excluding this front page.

Instructions

1. Answer **ALL** questions.
2. Write your student number on each page.
3. Marks for different sections are shown on the right-hand margin.
4. Clearly show your reasoning.
5. Non-programmable calculators may be used.

Question 1[28 Marks]

- (a) (i) State the purpose of biasing in transistors. [1 mark]
- (ii) Write down the equation for the drain current of a JFET/D-MOSFET device. Describe what each of the parameters in the equations represent. [4 marks]
- (iii) Using the equation in (ii) derive the expression for transconductance of a JFET/D-MOSFET. Show all your steps. [4 marks]
- (b) For the network shown in Fig Q1(b), determine the values of R_D and R_S that will result in a gain of -8. For the device $I_{DSS} = 10\text{mA}$, $V_P = -4\text{V}$, $V_{GS} = -1\text{V}$, $y_{os} = 20\mu\text{S}$ and $g_{mo} = 5\text{mS}$. Assume all capacitors to be extremely large. [10 marks]

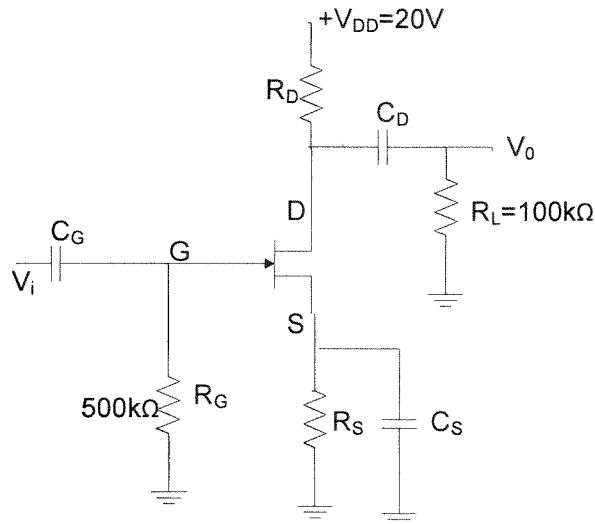


Fig. Q1(b)

- (c) (i) Sketch the circuit of a 555-timer connected as an astable multivibrator for operation at 500kHz, and hence determine the value of the capacitor needed using $R_A = R_B = 10\text{ k}\Omega$. [5 marks]
- (ii) Sketch the input and output waveforms of the astable multi vibrator circuit. [4 marks]

Question 2 [26 marks]

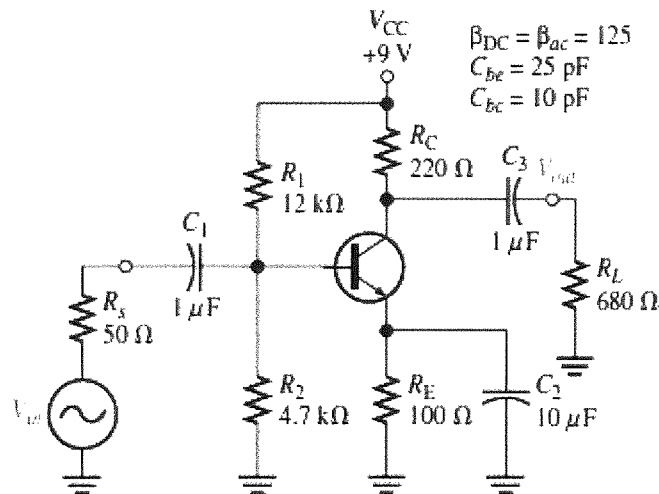


Fig Q2

- (a)
 - (i) List the capacitances that affect the circuit of Fig Q2 in low frequency region and the ones that affect it in the high frequency region. Explain your answer. [4 marks]
 - (ii) The midrange voltage gain of a certain amplifier is 65. At a certain frequency beyond midrange, the gain drops to 25. What is the gain reduction in dB? [3 marks]
- (b)
 - (i) Determine the critical frequencies associated with the low-frequency response of the BJT amplifier in Fig Q2. Which one is the dominant critical frequency? [10 marks]
 - (ii) Sketch the Bode plot. [3 marks]
- (c) Determine the voltage gain of the amplifier in FigQ2 at
 - (i) One-tenth of the dominant critical frequency, i.e. $0.1f_c$. [2 marks]
 - (ii) The dominant critical frequency, i.e. f_c . [2 marks]
 - (iii) Ten times the dominant critical frequency for the low-frequency response, i.e. $10f_c$. [2 marks]

Question 3 [20 marks]

- (a) The common mode input to a certain differential amplifier, having differential gain of 125 is $4\sin\pi t$ Volts. Calculate the common mode output if CMRR is 60dB. [5 marks]
- (b) Given a differential amplifier with the following parameters, CMRR = 80 dB, $A_d = 10^5$, $V_{in1} = 3\text{mV}$, $V_{in2} = 2.99\text{ mV}$, calculate the output voltage of the op-amp. Assume V_{in1} as the inverting input and V_{in2} as non-inverting input. [6 marks]

(c) (i) Operational amplifiers can be used to form various types of controlled sources. Mention four types of controlled sources. [4 marks]

(ii) Calculate the lower and upper cutoff frequencies of the bandpass filter circuit in Fig Q3. [5 marks]

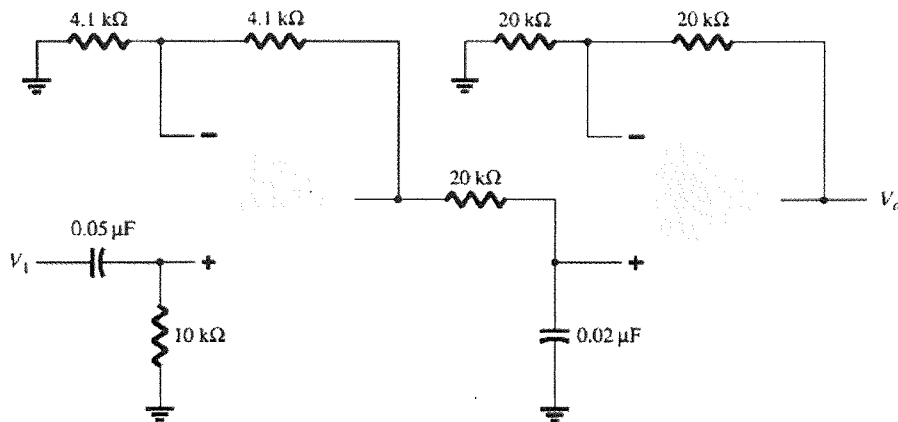


Fig Q3

Question 4 [26 Marks]

- (a) A class B, push pull amplifier drives a load of 16Ω , connected to the secondary of an ideal transformer. The supply voltage is $25V$. If the number of turns on the primary is 200 and the number of turns on the secondary is 50, calculate:
- (i) Maximum power output. [3 marks]
 - (ii) D.C input power [3 marks]
 - (iii) Efficiency [3 marks]
 - (iv) Maximum power dissipation per transistor [3 marks]
- (b) (i) In a power supply, explain the purpose of the rectifier, filter and regulator. [6 marks]
- (ii) Calculate the ripple factor of a sinusoidal signal having peak ripple of $2V$ on an average of $50V$. [4 marks]
- (iii) Given that a filter circuit produces an output of $18V$ unloaded and $22V$ under full load operation. Calculate the percentage voltage regulation. [4 marks]